

Entry: 001 **Date:** 1/27/2011 **Version:** 1.00 **Title:** Defining requirements

After the overwhelming success of the Class-D audio amplifier, it was decided to pursue an improved, less experimental version. Some ideas for the revised circuit include using entirely surface mount parts (reduced size and potentially increased performance), a higher supply voltage (increased power output), and an output inductor with a lower series resistance.

Other ideas brought forward for consideration are the use of a different class, such as Class G, Class H, Class I, or Class T. These ideas were rejected due to potential copyright/patent issues and complexity.

Entry: 002 **Date:** 1/29/2011 **Version:** 1.00 **Title:** Initial BOM

This post is duplicated from the NBitWonder Forums.

After some research, I've arrived at a partial bill of materials.

- MOSFETs - DMN4009
- Gate driver - IRS2004
- Comparator - LM311
- Integrating error amp - TL082

The amplifier will, like the prototype, be a self-oscillating type. My hope is that with proper construction techniques, the operating frequency will be quite high, ideally upwards of 500kHz. To that end, the output filter has been designed as a second-order Butterworth filter with a cutoff of 50kHz when operated with an 8-ohm speaker, a common value for home use. An inductor has been identified with a very low series resistance, which should help efficiency improve over the prototype.

The MOSFETs selected for use this time are cheaper than the IRL520Ns used last time and have a much lower on-state resistance, which should lead to increased efficiency. The MOSFET gate driver is cheaper than the one used for the experiment, but supports a lower drive current and a lower maximum voltage – but at the voltages slated for use in this project, this becomes a non-issue.

The input stages (TL082 and LM311) are slated to be unchanged from the previous iteration, since the parts are already low-cost and well-suited for the task at hand.

Expected power output, based on a +/-18V supply and an 8-ohm speaker, is $\frac{18^2}{8 \times 2} = 20W$ RMS under ideal conditions. Peak power (ie, turning on one MOSFET or the other and allowing the output filter to reach steady state) is arrived at with $\frac{V^2}{R}$; the extra factor of 2 converts peak power to RMS. To support this power output, the power supply should be capable of delivering $\sqrt{\frac{20W}{8\Omega}} = 1.58$ amps per channel.

Entry: 003 Date: 1/30/2011 Version: 1.00 Title: PCB Layout
--

Today saw significant work on the PCB layout.

Entry: 004 Date: 1/31/2011 Version: 1.00 Title: More PCB Layout

The PCB layout was finished today. A secondary version was created that features RCA input jacks instead of the more compact and lower cost 3.5mm stereo minijack.

Entry: 005 Date: 3/5/2011 Version: 1.00 Title: Prototype tweaks

While waiting for the PCBs to come in, I worked on the breadboarded prototype a little bit. I discovered that by changing the resistor and capacitor in the integrating feedback loop to 1M and 0.001uF respectively, power output increased greatly before audible distortion set in. Thankfully, implementing this on the PCB does not require any changes in the layout.

Entry: 006 Date: 3/6/2011 Version: 1.00 Title: Continued prototype work

Today, I constructed a duplicate amplifier circuit on the breadboard to have stereo capability, making sure to incorporate the changes from yesterday. Testing with my laptop as a signal source produced good results, though it seems that clipping sets in at a lower level now. My theory as to the cause is that the power supply I am using for testing cannot supply enough current to run both stereo channels at a high volume simultaneously.

With the 'laptop test' complete, I moved the amp to the living room to try it with my TV. Upon powering on the circuit, a loud 60Hz buzz permeated the room. It was determined that the cause of the buzz was a ground loop – the TV and amp were both grounded, and the signal cable between them also had a ground connection. Removing the AC ground from the power supply used on the amplifier solved the problem by eliminating all directly-connected paths between the two circuit grounds.

Entry: 007 Date: 3/10/2011 Version: 1.00 Title: PCBs Arrive

The PCBs arrived today!

Rather than dive right in with their assembly, though, I decided to spend some time focusing on the amplifier's packaging. As this is an area I have yet to pay any real attention to on any of my projects, I thought it appropriate to make it a priority for this project. A brief trip to Radio Shack left me with some 4-40 mounting hardware (nuts, bolts, and washers), a 3x5x7 inch plastic project enclosure, a panel-mount audio input jack, and spring-loaded speaker terminals. A few hours spent with a Dremel tool left me with suitably sized holes in the enclosure.

Entry: 008 Date: 3/11/2011 Version: 1.00 Title: Power supply assembly

Today saw much of the amplifier's power supply assembly. The transformer was mounted in

the case, along with the power switch, fuse, and line input cord. The appropriate connections were soldered, and the supply was tested. The 24V center-tapped transformer that was selected for this build produced a no-load voltage of 13.6VAC from the center tap to each end of the secondary winding. As this voltage when rectified and filtered will exceed the voltage limits of at least one of the analog components, it may be necessary to drop the voltage slightly with diodes or an add-on regulator if the voltage does not drop appreciably under load.

I also began assembling the main amplifier PCB, but was forced to an abrupt end when I discovered that I made a mistake in the parts order, procuring one too few comparators and the wrong value of output filter capacitors. A parts order was placed with Newark for the missing components.

Entry: 009 Date: 3/12/2011 Version: 1.00 Title: More PCB assembly work
--

The PCB was built up to the extent possible today. Still not populated are the various input and output connections (as these are more easily done once mounted in the case), the power filtering capacitors (as they are large and would likely impede access to the smaller-footprinted components).

In light of the unexpectedly high transformer secondary voltage discovered yesterday, some work was done to identify a better way of powering the amplifier. An inexpensive switch-mode controller, the AP34063, was found to be a sub-one-dollar solution to the problem. In a future revision of the amplifier, a single-ended supply of up to 40VDC (or 28VAC followed by a rectifier) will be applied to the amplifier PCB and sent directly to the output MOSFETs. This input voltage will also pass through a low-current switchmode regulator centered on the aforementioned AP34063 which will generate a 12VDC control supply to operate the input stages and MOSFET gate driver IC. This will allow for a greater supply voltage, boosting output power; additionally, the power supply requirements will be greatly relaxed.

Entry: 010 Date: 3/13/2011 Version: 1.00 Title: Single-supply amplifier

An initial design was drawn up for the single-supply amplifier. It is now included in the github repository for the project, though it is far from done.